

Sai Kathika saiprem@ucsb.edu
Pete Makrygiannis pmakrygiannis@ucsb.edu
Rahul Varghese rvarghese@ucsb.edu

ECE 154A Lab 4

1. a. Please indicate how many hours you spent on this lab.

Spent a total of 30 hours

b. A completed version of Table 1.

| Cycle | reset | pc | Instr | branch | srca | srcb | alurest | zero | pcsrc | Writedata | memwrite | read data |
|-------|-------|----|--------------------------------|--------|------|------|---------|------|-------|-----------|----------|-----------|
| 1 | 1 | 00 | addi \$2,\$0,5 20020005 | 0 | 0 | 5 | 5 | 0 | 0 | 0 | 0 | x |
| 2 | 0 | 04 | addi \$3,\$0,12 2003000c | 0 | 0 | c | c | 0 | 0 | 0 | 0 | x |
| 3 | 0 | 08 | addi \$7,\$3,-9 20067fff7 | 0 | C | -9 | 3 | 0 | 0 | 0 | 0 | x |
| 4 | 0 | 0C | or \$4,\$7,\$2 00e22025 | 0 | 3 | 5 | 7 | 0 | 0 | 5 | 0 | x |
| 5 | 0 | 10 | and \$5,\$3,\$4 00642824 | 0 | C | 7 | 4 | 0 | 0 | 7 | 0 | x |
| 6 | 0 | 14 | add \$5,\$5,\$4 00a42820 | 0 | 4 | 7 | B | 0 | 0 | 7 | 0 | x |
| 7 | 0 | 18 | beq \$5,\$7,end 10a7000a | 1 | B | 3 | 8 | 0 | 0 | 3 | 0 | x |
| 8 | 0 | 1C | slt \$4,\$3,\$4 0064202a | 0 | C | 7 | 0 | 1 | 0 | 7 | 0 | x |
| 9 | 0 | 20 | beq \$4,\$0,around 10800001 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | x |
| 10 | 0 | 28 | slt \$4,\$7,\$2 00e2202a | 0 | 3 | 5 | 1 | 0 | 0 | 5 | 0 | x |
| 11 | 0 | 2C | add \$7,\$4,\$5 00853820 | 0 | 1 | B | C | 0 | 0 | B | 0 | x |
| 12 | 0 | 30 | sub \$7,\$7,\$2 00e23822 | 0 | C | 5 | 7 | 0 | 0 | 5 | 0 | x |
| 13 | 0 | 34 | sw \$7,68(\$3) ac670044 | 0 | C | 44 | 50 | 0 | 0 | 7 | 1 | x |
| 14 | 0 | 38 | lw \$2,80(\$0) 8c020050 | 0 | 0 | 50 | 50 | 0 | 0 | 5 | 0 | 7 |
| 15 | 0 | 3C | j end 08000011 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | x |
| 16 | 0 | 44 | sw \$2,84(\$0) ac020054 | 0 | 0 | 54 | 54 | 0 | 0 | 7 | 1 | x |

c. An image of the simulation waveforms showing correct operation of the processor.

Our group spent a lot of time trying to get modelsim to output the waveforms, but we were unable to.

Everything compiled correctly without any errors but the waveforms were not what we anticipated from the code we wrote.

ModelSim PE Student Edition 10.4a

File Edit View Compile Simulate Add Transcript Tools Layout Bookmarks Window Help

100 ns

Layout Simulate ColumnLayout AllColumns

Objects

Instance

- adder
- ALU
- aludec
- controller
- datapath
- dmem
- flpr
- imem
- mandec
- mips
- mux2
- regfile
- siz
- tb
- top
- vsim_capacity#

Names (Active)

- RASSIGN#21
- RASSIGN#6
- RASSIGN#7
- RASSIGN#17
- RASSIGN#10
- RASSIGN#21
- RASSIGN#27
- RASSIGN#21
- RASSIGN#45

Library List

Transcript

```


# Time: 0 ns Iteration: 0 Instance: /top/mips/dp/pcadd2 File: C:/Users/Rahul Varghese/Desktop/lab4/mips.v
# ** Warning: (vsim-3015) C:/Users/Rahul Varghese/Desktop/lab4/mips.v(70): [PCDFC] - Port size (32) does not match connection size (1) for port 'b'. The port definition is at: C:/Users/Rahul Varghese/Desktop/lab4/mips.v(10).
# Compile of testbench.v was successful.
# Compile of mips.v was successful.
# Compile of mipsmem.v was successful.
# Compile of mips.v was successful.
# Compile of datapath.v was successful.
# Compile of controller.v was successful.
# Compile of ALU.v was successful.
# 7 compiles, 0 failed with no errors.

```


VSIM 25>

Project: lab4 Now: 0 ns Delta: 0 top

| Name | Status | Type | Order | Modified |
|--------------|--------|---------|-------|----------|
| memfile2.dat | | .dat... | - | 11/13/20 |
| mipsmem.v | ✓ | Verilog | 2 | 11/14/20 |
| mipstop.v | ✓ | Verilog | 3 | 11/15/20 |
| mips.v | ✓ | Verilog | 1 | 11/14/20 |
| tb.v | ✓ | Verilog | 0 | 11/15/20 |
| memfile.dat | | .dat... | - | 11/12/20 |
| alu.v | ✓ | Verilog | 4 | 11/12/20 |

 

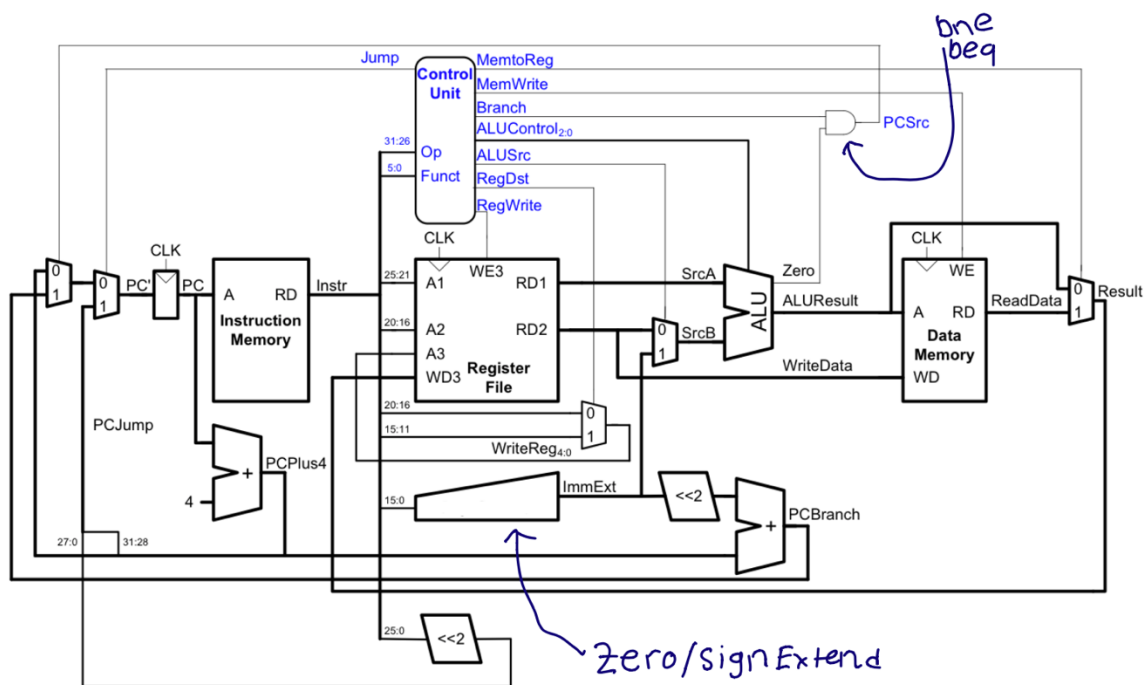d. Marked up versions of the datapath schematic and decoder tables that add the ori and bne instructions.



Single-cycle MIPS processor

e. Your Verilog code for your modified MIPS processor

controller.v

```

always @*
  case(op)
    6'b000000: controls <= 9'b110000010; // RTYPE
    6'b100011: controls <= 9'b101001000; // LW
    6'b101011: controls <= 9'b001010000; // SW
    6'b000100: controls <= 9'b000100001; // BEQ
    6'b001000: controls <= 9'b101000000; // ADDI
    6'b000010: controls <= 9'b000000100; // J

    // CHANGES START
    // added functionality of ORI and BNE to opcodes
    6'b001101: controls <= 9'b101000011; // ORI
    6'b000101: controls <= 9'b000100001; // BNE
    // CHANGES END

    default: controls <= 9'bxxxxxxxx; // Not found, illegal
  endcase
endmodule

```

```

always @*
  case(aluop)
    2'b00: alucontrol <= 3'b010;

    // CHANGES START
    // added beq and ori
    // included sub needed to beq
    2'b01: alucontrol <= 3'b110;
    2'b11: alucontrol <= 3'b001;
    // CHANGES END

    default: case(func) // R-type instructions
      6'b100000: alucontrol <= 3'b010; // add
      6'b100010: alucontrol <= 3'b110; // sub
      6'b100100: alucontrol <= 3'b000; // and
      6'b100101: alucontrol <= 3'b001; // or
      6'b101010: alucontrol <= 3'b111; // slt
      default: alucontrol <= 3'bxxx; // ???
    endcase
  endcase
endcase

```

Datapath.v

```
// CHANGES START
// make changes to include functionality for both
// 0 and sign extend
module extend (input [15:0] a,
              input [2:0] alucontrol,
              input regdst,
              output [31:0] y);
  assign y = (alucontrol == 3'b001 & regdst == 0) ? {{16'b0}, a} : {{16{a[15]}}, a};
endmodule
// CHANGES END
```

Mips.v

```
// CHANGES START
// add bne functionality
assign pcsrc = (op == 6'b000101) ? branch & ~zero : branch & zero;
// CHANGES END: here
```

```
// **PUT YOUR CODE HERE**
wire [4:0] writereg;
wire [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
```

```
// CHANGES START
wire [31:0] imm, signimmsh;
// CHANGES END
```

```
//CHANGES START
extend ext(instr[15:0], alucontrol[2:0], regdst, imm);
mux2 #(32) srcbmux(writedata, imm, alusrc, srcb); // replaced signimm with imm
//CHANGES END
```

Mipsmem.v

```
// CHANGES START
$readmemh("memfile2.dat", RAM);
// CHANGES END
```

Mipstop.v

```
// CHANGES START
module top (input clk, reset,
            output [31:0] writedata, dataadr,
            output memwrite);

    wire [31:0] pc, instr, readdata;
    // CHANGES END
```

Memfile2.dat

```
1  34088000
2  20098000
3  350a8001
4  11090005
5  0128582a
6  15600001
7  08000001
8  01485022
9  350800ff
10 016a5820
11 01484022
12 ad680052
```

f. Completed version of Tables 2 and 3 for the modified MIPS processor.

Table 2. Extended functionality for the main decoder:

| Instruction | Op _{5:0} | RegWrite | RegDst | AluSrc | Branch | MemWrite | MemtoReg | ALUOp _{1:0} | Jump |
|-------------|-------------------|----------|--------|--------|--------|----------|----------|----------------------|------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 | 0 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 | 0 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 | 0 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 | 0 |
| addi | 001000 | 1 | 0 | 1 | 0 | 0 | 0 | 00 | 0 |
| j | 000010 | 0 | X | X | X | 0 | X | XX | 1 |
| ori | 001101 | 1 | 0 | 1 | 0 | 0 | 0 | 00 | 0 |
| bne | 000101 | 0 | X | 0 | 1 | 0 | X | 01 | 0 |

Table 3. Extended functionality for the ALU decoder:

| ALUOp _{1:0} | Meaning |
|----------------------|---------------------|
| 00 | Add |
| 01 | Subtract |
| 10 | Look at funct field |
| 11 | Ori |

g. The contents of your memfile2.dat containing your test2 machine language code.

```


1  34088000
2  20098000
3  350a8001
4  11090005
5  0128582a
6  15600001
7  08000001
8  01485022
9  350800ff
10 016a5820
11 01484022
12 ad680052

```

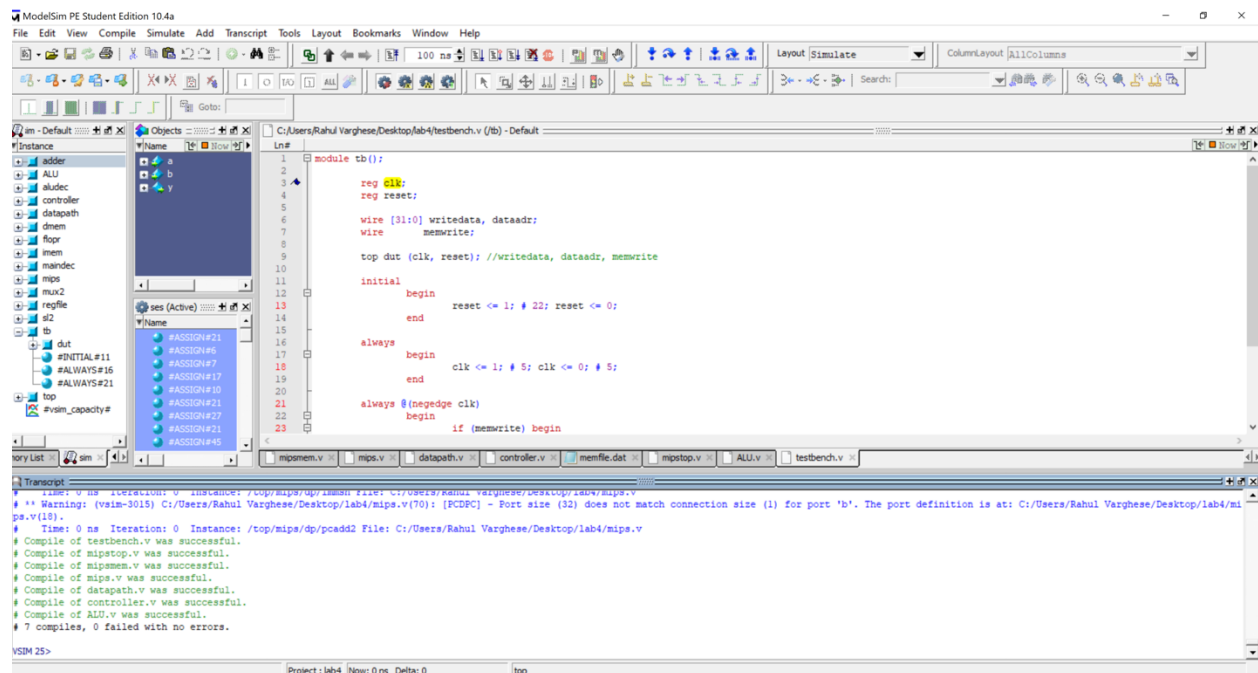
h. An image of the simulation waveforms showing correct operation of your modified processor on the new program. What address and data value are written by the sw instruction?

Our group spent a lot of time trying to get modelsim to output the waveforms, but we were unable to.

Everything compiled correctly without any errors but the waveforms were not what we anticipated from the code we wrote.



| Name | Status | Type | Order | Modified |
|--------------|--------|---------|-------|----------|
| memfile2.dat | | .dat... | - | 11/13/20 |
| mipsmem.v | ✓ | Verilog | 2 | 11/14/20 |
| mipstop.v | ✓ | Verilog | 3 | 11/15/20 |
| mips.v | ✓ | Verilog | 1 | 11/14/20 |
| tb.v | ✓ | Verilog | 0 | 11/15/20 |
| memfile.dat | | .dat... | - | 11/12/20 |
| alu.v | ✓ | Verilog | 4 | 11/12/20 |

 

BOX Code

There is folder before changes which is the code before the changes implemented

There is folder after changes which is the code after the changes implemented

<https://ucsb.box.com/s/2bfy4169vd3xvosai0kqle5qbghw9h84>

